


6. Principske šeme SAU

6.1. Napisati funkcije prenosa:

- Linearnog i obrtnog potencijometra
- Tahogeneratora
- Pojačavača snage


Rešenje:

a) Linearni potencijometar

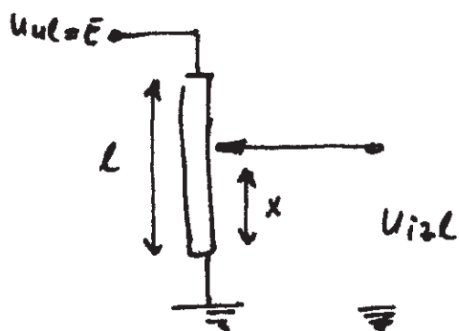

$$x \in [0, l] \quad U_{izl} = \frac{x}{l} U_{ul} = \frac{x}{l} E$$

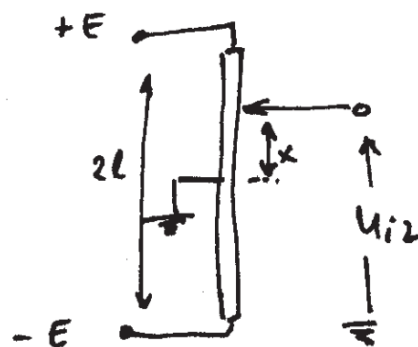
$$G(s) = \frac{U_{izl}(s)}{X(s)} = \frac{E}{l} = k_p$$



$$x \in [-l, l] \quad U_{izl} = \frac{x}{l} U_{ul} = \frac{x}{l} E$$


$$G(s) = \frac{U_{izl}(s)}{X(s)} = \frac{E}{l} = k_p$$

Obrtni potencijometar

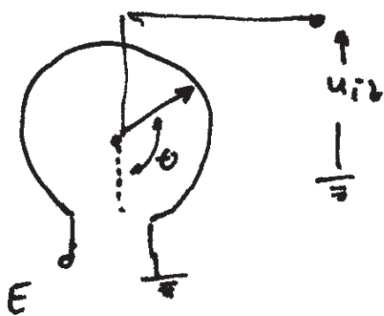

$$\theta \in [0, 2\pi] \quad U_{izl} = \frac{\theta}{2\pi} E$$

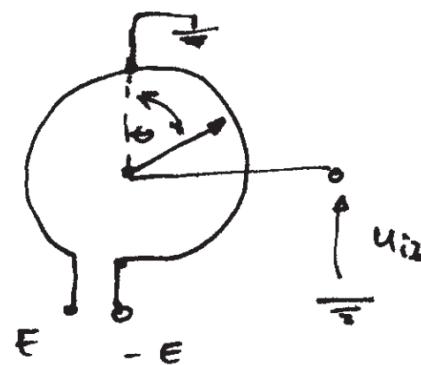
$$G(s) = \frac{U_{izl}(s)}{\theta(s)} = \frac{E}{2\pi} = k_p$$




$$\theta \in [-\pi, \pi] \quad U_{izl} = \frac{\theta}{\pi} E$$

$$G(s) = \frac{U_{izl}(s)}{\theta(s)} = \frac{E}{\pi} = k_p$$

b) Tahogenerator

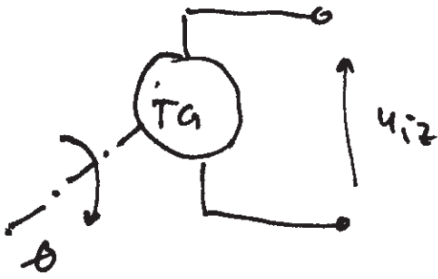

c) Pojačavač snage

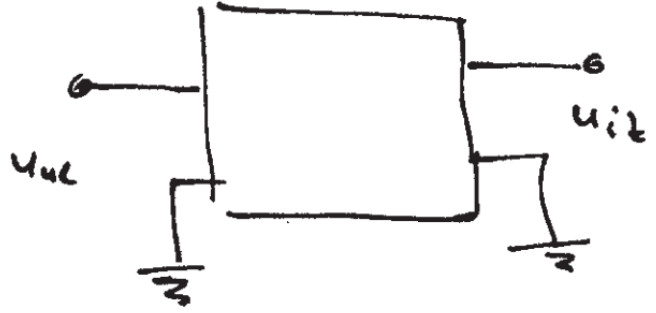


$$U_{izl} = k_{tg} \omega \quad G_{\omega}(s) = \frac{U_{izl}(s)}{\omega(s)} = k_{tg}$$

$$U_{izl} = k_{tg} \dot{\theta} = k_{tg} s \theta(s) \quad G_{\theta}(s) = \frac{U_{izl}(s)}{\theta(s)} = s k_{tg}$$


$$G(s) = \frac{U_{izl}(s)}{U_{ul}(s)} = K_{PS}$$

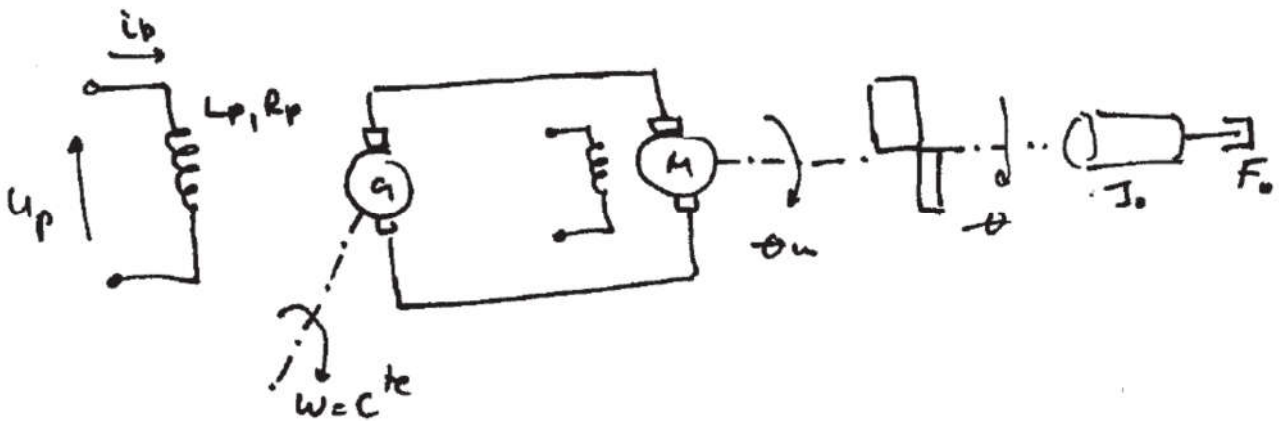6.2. Odrediti funkciju prenosa $W(s) = \frac{\theta_m(s)}{U_p(s)}$ sistema sa slike (Vard-Leonardova grupa):



Rešenje:

Ekvivalentna električna šema:

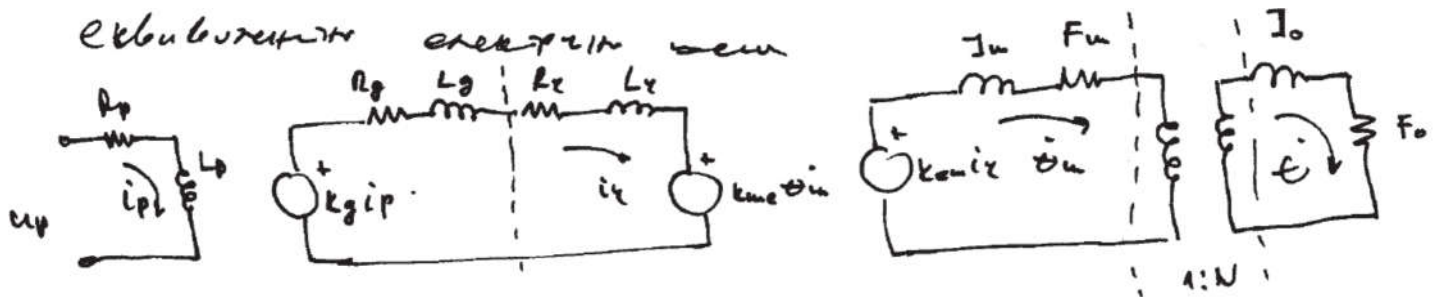

$$\dot{\theta}_m = N \dot{\theta} \quad J = J_m + \frac{J_o}{N^2} \quad F = F_m + \frac{F_o}{N^2}$$

$$(R_p + sL_p) I_p(s) = U_p(s)$$

$$-k_g I_p(s) + [(L_r + L_g)s + R_r + R_g] I_r(s) + k_m \dot{\theta}_m(s) = 0$$

$$-k_{em} I_r(s) + (Js + F) \dot{\theta}_m(s) = 0$$

$$L_g, L_r \approx 0$$

$$G(s) = \frac{\theta_m(s)}{U_p(s)} = \frac{\dot{\theta}_m(s)}{sU_p(s)} = \frac{\Delta_{13}(s)}{s\Delta(s)}$$


$$\Delta(s) = \begin{vmatrix} R_p + sL_p & 0 & 0 \\ -k_g & R_r + R_g & k_{me} \\ 0 & -k_{em} & Js + F \end{vmatrix}$$

$$G(s) = \frac{k_g k_{em}}{s(R_p + sL_p)[(R_r + R_g)(Js + F) + k_{em}k_{me}]} = \frac{k}{s(1 + sT_1)(1 + sT_2)}$$

$$k = \frac{k_g k_{em}}{R_p [(R_r + R_g)F + k_{em}k_{me}]} \quad T_1 = \frac{L_p}{R_p} \quad T_2 = \frac{(R_r + R_g)J}{[(R_r + R_g)F + k_{em}k_{me}]}$$

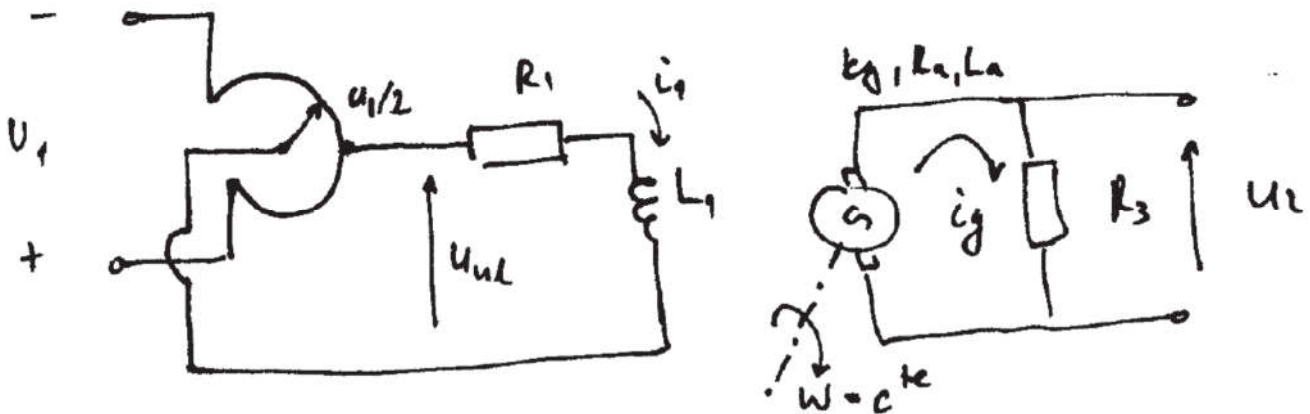6.3. Nacrtati strukturni blok dijagram i naći funkciju prenosa generatora prikazanog na slici. Ulazni signal je ugao obrtanja potenciometra θ_1 , a izlaz je napon u_2 na opterećenju. Parametri sistema su:

$$k_g = 1000 \frac{V}{A}; R_1 = 1k\Omega; L_1 = 10H; L_a = 0.1H; R_a = 1\Omega; U_1 = 50V; \theta_{\max} = 2.285rad; R_3 = 9\Omega$$




Rešenje:

$$\text{Potenciometar: } U_{ul} = k_p \theta \quad k_p = ? \quad \frac{U_1}{2} = k_p \theta_{\max} \Rightarrow k_p = \frac{U_1}{2\theta_{\max}}$$

$$\text{Pobudno kolo: } U_{ul} = L_1 \frac{di_1}{dt} + R_1 i_1 \Rightarrow I_1(s) = \frac{U_{ul}(s)}{R_1 + sL_1}$$

$$\text{Generator: } u_g = k_g i_1 \Rightarrow U_g(s) = k_g I_1(s); \quad u_g = L_a \frac{di_a}{dt} + (R_a + R_3) i_g \Rightarrow I_g(s) = \frac{U_g(s)}{R_a + R_3 + sL_a}$$
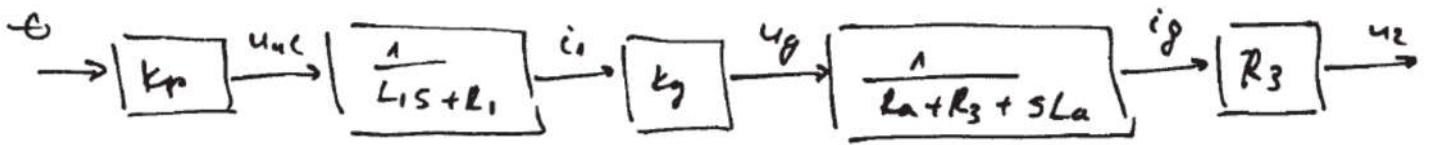
$$\text{Izlaz: } u_2 = R_3 i_g \Rightarrow U_2(s) = R_3 I_g(s)$$




$$\frac{U_2(s)}{\theta(s)} = \frac{k_p k_g R_3}{(L_1 s + R_1)(L_a s + R_a + R_3)} = \frac{\frac{k_p k_g R_3}{R_1(R_a + R_3)}}{\left(1 + \frac{L_1}{R_1} s\right) \left(1 + \frac{L_a}{R_a + R_3} s\right)} = \frac{k}{(1 + sT_1)(1 + sT_2)}$$

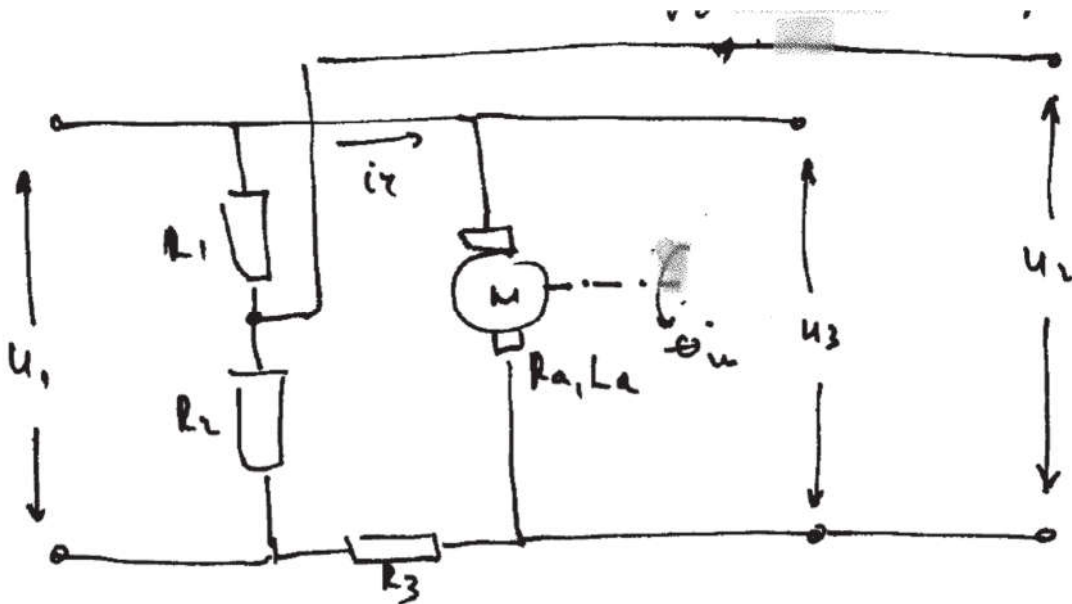6.4. Na slici je prikazan sistem za merenje brzine obrtanja motora jednosmerne struje. Odrediti funkciju prenosa

$W(s) = \frac{U_2(s)}{\dot{\theta}_m(s)}$. Parametri sistema su: $k_{me} = 0.105 \frac{V}{\text{ob/min}}$; $R_1 = R_2 = 100\Omega$; $R_a = 2\Omega$; Odrediti otpornost R_3 iz

uslova ravnoteže $u_2 = 0$, kada je motor zakočen. Zanemariti induktivnost rotora motora L_a .



$$\dot{\theta}_m = \omega$$

$$u_1 = L_a \frac{di_r}{dt} + R_a i_r + k_{me} \omega + R_3 i_r$$

$$u_2 = \frac{R_2}{R_1 + R_2} u_1 - R_3 i_r$$

$$u_2 = \frac{R_2}{R_1 + R_2} L_a \frac{di_r}{dt} + \frac{R_2(R_a + R_3)}{R_1 + R_2} i_r + \frac{R_2}{R_1 + R_2} k_{me} \omega - R_3 i_r$$

$$u_2 = \frac{R_2}{R_1 + R_2} L_a \frac{di_r}{dt} + \frac{R_a R_2 - R_1 R_3}{R_1 + R_2} i_r + \frac{R_2}{R_1 + R_2} k_{me} \omega$$

$$L_a = 0 \Rightarrow u_2 = \frac{R_a R_2 - R_1 R_3}{R_1 + R_2} i_r + \frac{R_2}{R_1 + R_2} k_{me} \omega$$


$$\omega = 0 \Rightarrow u_2 = 0 \Rightarrow R_a R_2 = R_1 R_3 \Rightarrow R_3 = \frac{R_a R_2}{R_1} = R_a = 2\Omega$$

$$u_2 = \frac{R_2}{R_1 + R_2} k_{me} \omega = \frac{1}{2} k_{me} \omega = 0.05025 \omega$$

$$W(s) = \frac{U_2(s)}{\omega(s)} = 0.05025$$

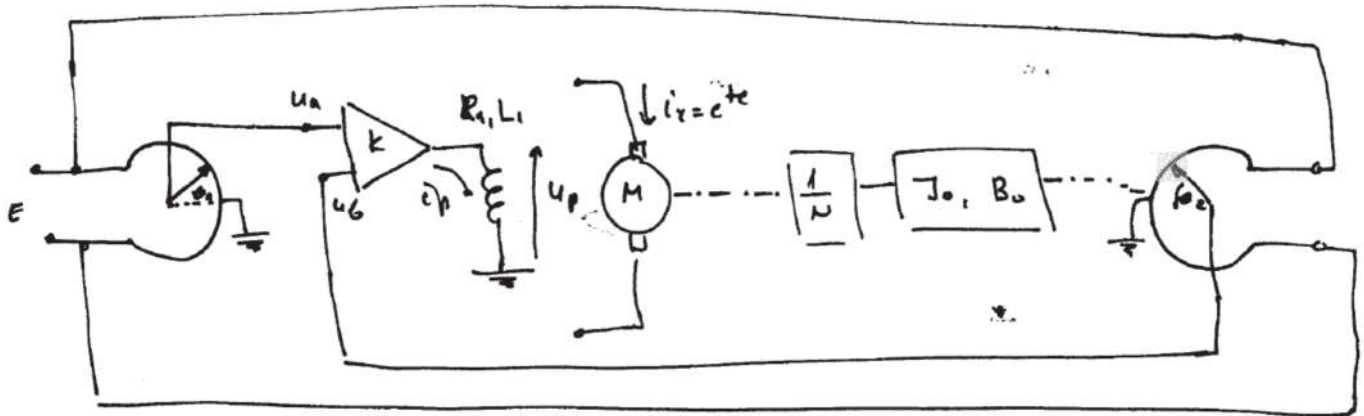6.5. Na slici je prikazan pozicioni servosistem. Formirati strukturnu blok šemu. Parametri sistema su:

$$J_m = 0.26 \cdot 10^{-3} \text{ kg} \cdot \text{m}^2; B_m = 65.5 \cdot 10^{-5} \text{ Nms}; k_{em} = 74.5 \cdot 10^{-3} \frac{\text{Nm}}{\text{A}}; N = 22.5; k_p = 1 \frac{\text{V}}{\text{rad}}; R_1 = 1 \text{ k}\Omega; L_1 = 5 \text{ H}; K = 2;$$



Rešenje:

Potenciometar: $u_a = k_p \theta_1$ $u_b = k_p \theta_2$

Pojačavač: $U_p = K(u_a - u_b)$



MJS upravljani strujom u pobudnom kolu:

$$u_p = R_1 i_p + L_1 \frac{di_p}{dt}; \quad u_r = R_r i_r + L_r \frac{di_r}{dt} + k_{me} \omega; \quad i_r = \text{const.}$$

$$J = J_m + \frac{J_o}{N^2}; \quad B = B_m + \frac{B_o}{N^2}$$

$$k_{em} i_p = J \frac{d\omega}{dt} + B\omega; \quad U_p(s) = (R_1 + sL_1) I_p(s) \Rightarrow \frac{I_p(s)}{U_p(s)} = \frac{1}{(R_1 + sL_1)}$$
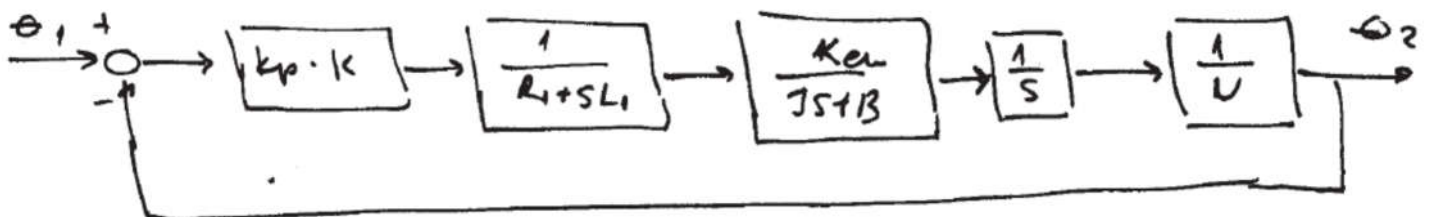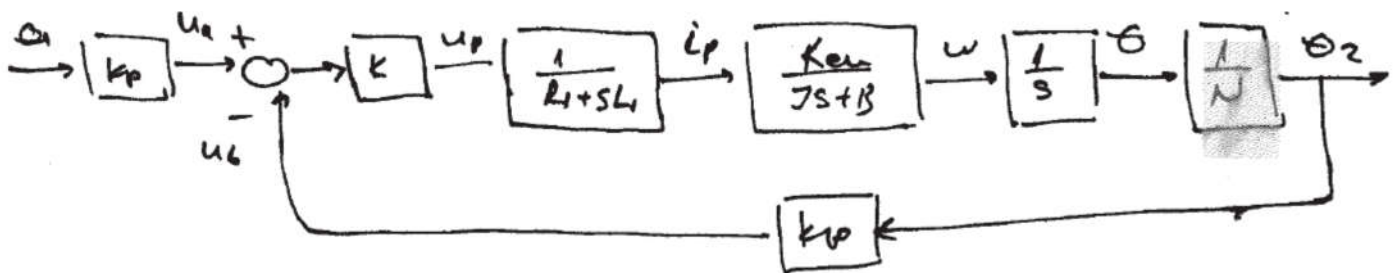
$$(Js + B)\omega(s) = \frac{k_{em}}{(R_1 + sL_1)} U_p(s) \Rightarrow \frac{\omega(s)}{U_p(s)} = G_m(s) = \frac{k_{em}}{(R_1 + sL_1)(Js + B)}$$




6.6. Formirati strukturnu blok šemu brzinskog servosistema prikazanog na slici. Parametri sistema su:

$$k_{me} = 0.105 \frac{V}{\text{ob/min}}; k_{em} = 0.001 \frac{Nm}{A}; J_m = 10^{-5} k_g m^2; J_o = 222 \cdot 10^{-3} k_g m^2;$$

$$F_m = F_o = 0; R_1 = R_2 = 100 \Omega; R_r = 2 \Omega; L_r = 0; R = 10 k\Omega; C = 10 \mu F.$$

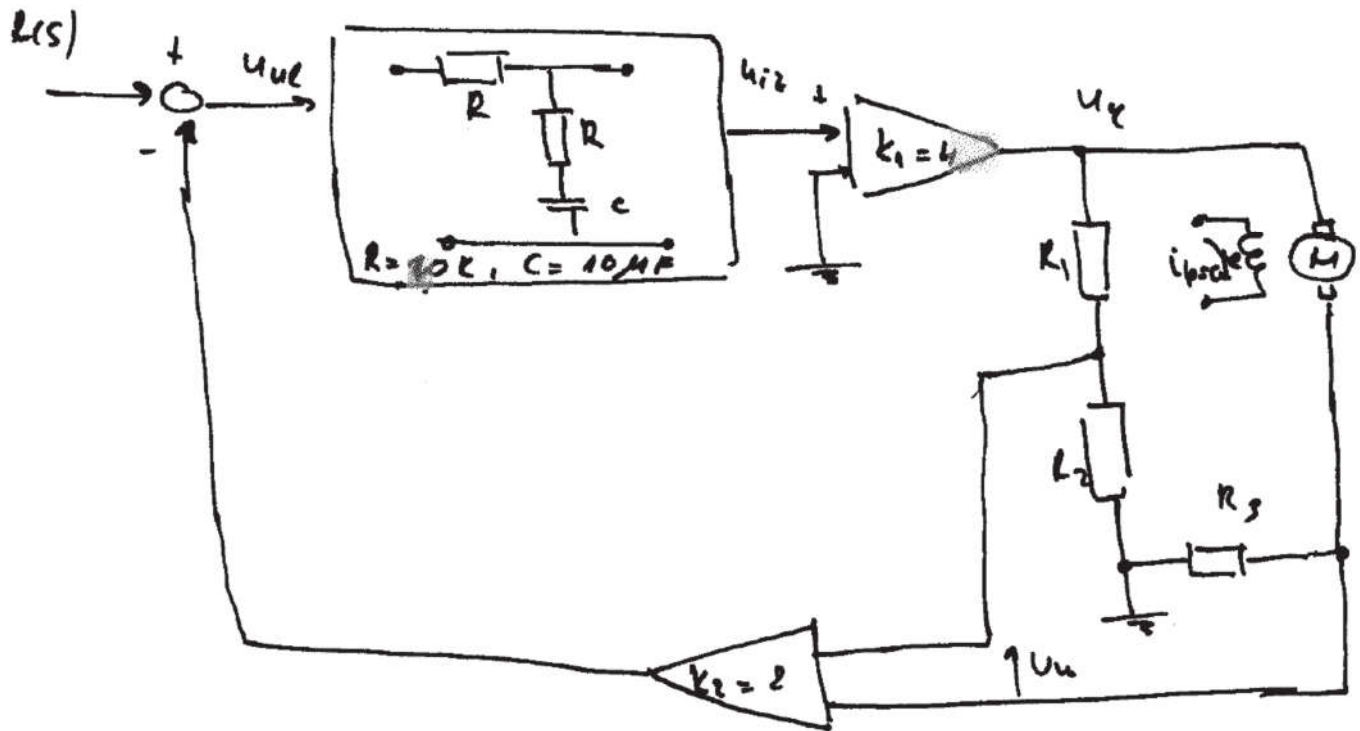Odrediti otpornost R_3 iz uslova da je napon $U_m = 0$ kada je $\omega = 0$.



Rešenje:

$$U_{iz} = \frac{R + \frac{1}{sC}}{2R + \frac{1}{sC}} U_{ul} = \frac{1 + sRC}{1 + s2RC} U_{ul}$$

Integralni kompenzator:

$$\frac{U_{iz}}{U_{ul}} = \frac{1 + sRC}{1 + s2RC} = \frac{1 + s0.1}{1 + s0.2} = \frac{1}{2} \frac{s + 10}{s + 5}$$

$$u_r = k_1 u_{iz} = 4 u_{iz} \quad u_r = L_r \frac{di_r}{dt} + R_r i_r + R_3 i_r + k_{me} \omega \Rightarrow i_r = \frac{u_r - k_{me} \omega}{R_r + R_3}$$

$$k_{em} i_r = J \frac{d\omega}{dt} + B \omega; \quad J = J_m + \frac{J_o}{N^2}; \quad B = B_m + \frac{B_o}{N^2}$$

$$0 = J \frac{d\omega}{dt} + B \omega + \frac{k_{em} k_{me} \omega}{R_r + R_3} - \frac{k_{em}}{R_r + R_3} u_r$$

Motor jednosmerne struje:

$$\frac{k_{em}}{R_r + R_3} U_r(s) = \left[(Js + B) + \frac{k_{em} k_{me}}{R_r + R_3} \right] \omega(s)$$

$$k_{em} U_r(s) = \left[(Js + B)(R_r + R_3) + k_{em} k_{me} \right] \omega(s)$$

$$\frac{\omega(s)}{U_r(s)} = \frac{k_{em}}{(Js + B)(R_r + R_3) + k_{em} k_{me}} = \frac{k_m}{1 + sT_m}$$

Tahometarski merni most:

$$u_m = \frac{R_2}{R_1 + R_2} u_r - R_3 i_r ; \quad u_r = (R_r + R_3) i_r + k_{me} \omega$$


$$u_m = \frac{R_2}{R_1 + R_2} [(R_r + R_3) i_r + k_{me} \omega] - R_3 i_r$$

$$u_m = \frac{R_r R_2 - R_1 R_3}{R_1 + R_2} i_r + \frac{R_2}{R_1 + R_2} k_{me} \omega$$


$$\omega = 0 \Rightarrow u_m = 0 \Rightarrow R_r R_2 = R_1 R_3 \Rightarrow R_3 = \frac{R_r R_2}{R_1} = R_r = 2\Omega$$

$$u_m = \frac{R_2}{R_1 + R_2} k_{me} \omega = \frac{1}{2} k_{me} \omega = 0.05025 \omega$$

$$\frac{U_m(s)}{\omega(s)} = 0.05025$$

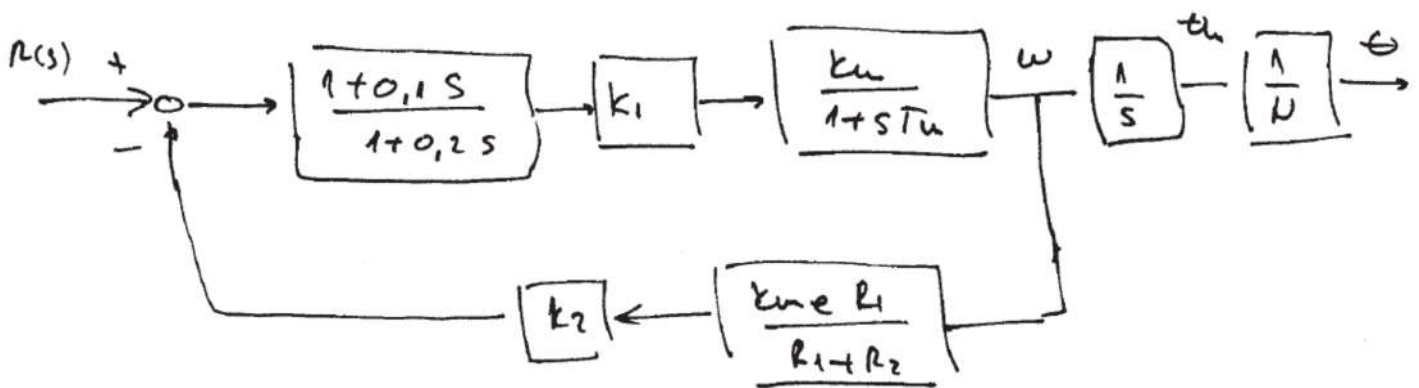

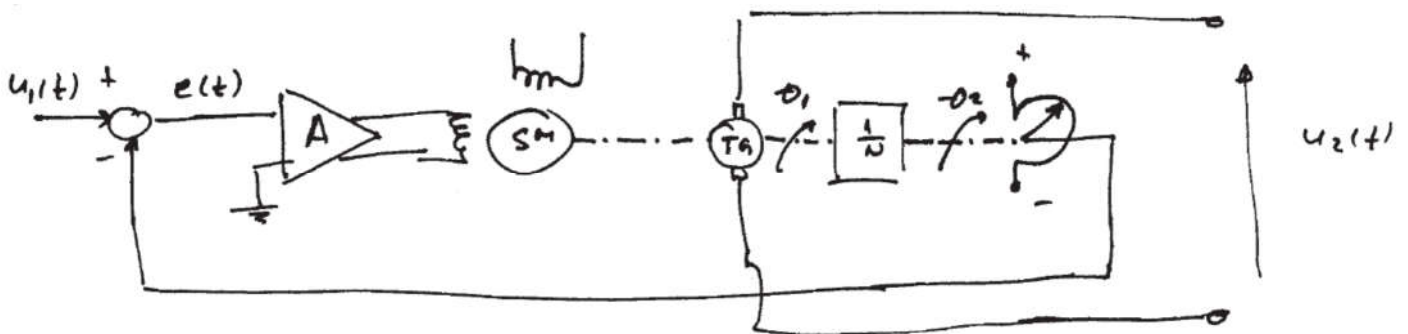6.7. Za servomehanizam sa slike ulaz je u_1 , a izlaz u_2 . Nacrtati strukturnu blok šemu i odrediti pojedinačno f-je prenosa elemenata sistema.



Rešenje:


Servo pojačavač: $W_{sp}(s) = A$

Mehanički reduktor: $W_{mr}(s) = \frac{\theta_2(s)}{\theta_1(s)} = \frac{1}{N}$

Servo motor: $W_{sm}(s) = \frac{\theta_1(s)}{U_m(s)} = \frac{k}{s(1+sT)}$

Potenciometar: $W_{pot}(s) = k_p$

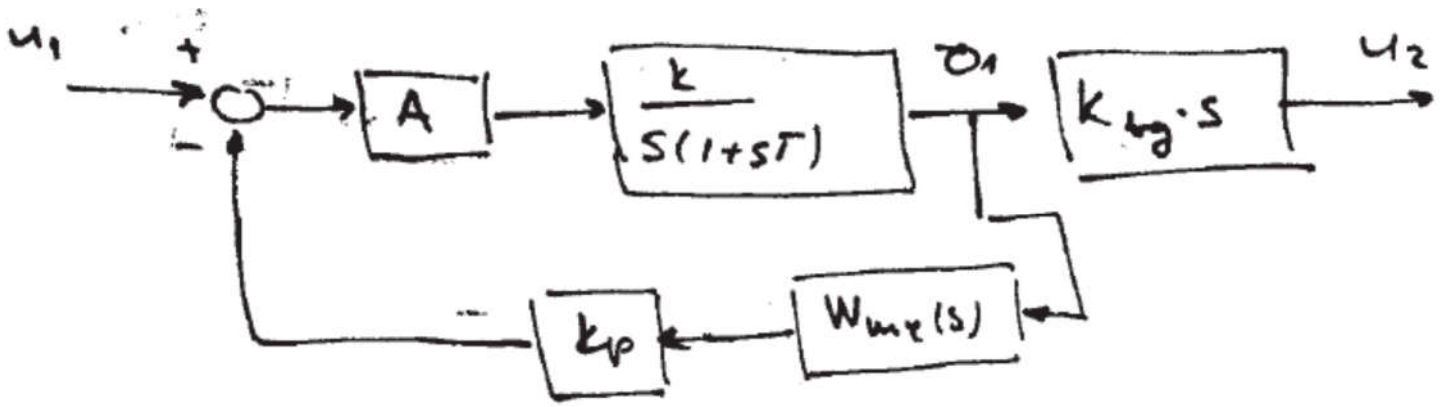
Tahogenerator: $W_{tg}(s) = \frac{U_2(s)}{\theta_1(s)} = sK_{tg}$



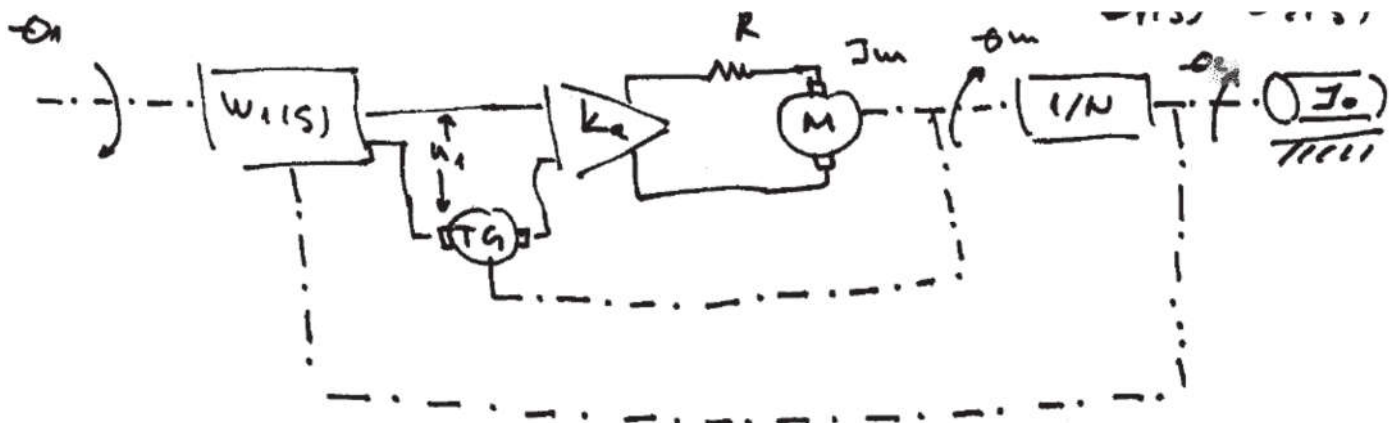6.8. Na slici je prikazana principska šema pratećeg sistema. Formirati strukturnu blok šema ako je poznato sledeće:

$$R = 1\Omega; K_a = 60; k_{me} = 0.75 \frac{V}{\text{rad/s}}; k_{em} = 0.5 \frac{Nm}{A}; J_m = 0.007 k_g m^2; J_o = 2880 k_g m^2; N = 100;$$

$$F_m = F_o = 0; L_r = 0; K_{tg} = 0.04 \frac{V}{\text{rad/s}}. \text{ Dok je } W_1(s) = \frac{U_1(s)}{\theta_1(s) - \theta_2(s)} = \frac{5}{1 + 0.025 \cdot s}.$$




Rešenje:

$W_1(s)$ – transformatorska veza selsina.

$$R I_r(s) + k_{me} s \theta_m(s) = U_a(s)$$

MJS upravljan strujom u rotorskom kolu: $-k_{em} I_r(s) + \left(J_m + \frac{J_o}{N^2} \right) s \theta_m(s) = 0$
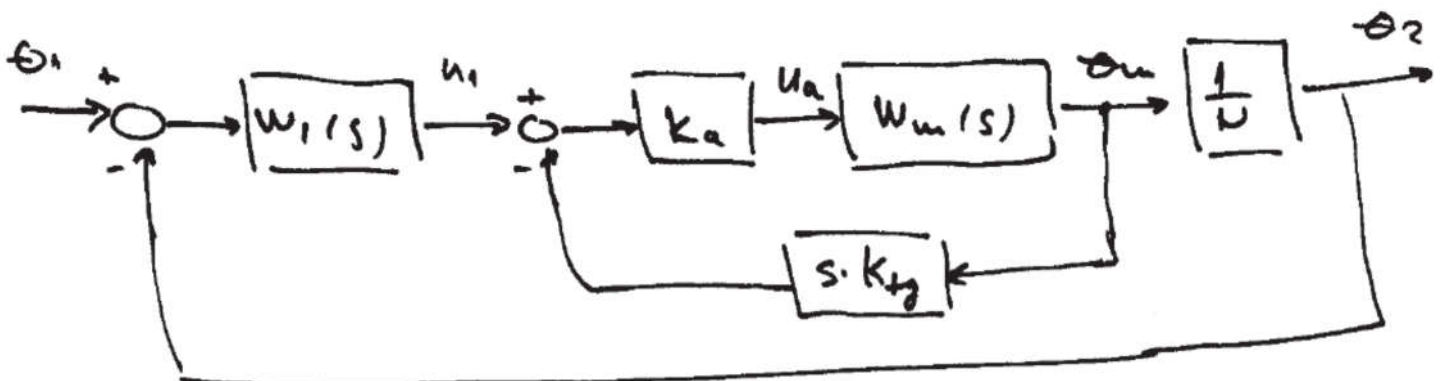
$$W_m(s) = \frac{\theta_m(s)}{U_a(s)} = \frac{k_{em}}{s \left[R \left(J_m + \frac{J_o}{N^2} \right) s + k_{em} k_{me} \right]}$$




6.9. Na slici je prikazan sistem za regulaciju brzine obrtanja jednosmernog motora. Parametri sistema su:


pojačanje motora $k_m = 0.5 \frac{\text{rad}}{\text{V} \cdot \text{s}}$; vremenska konstanta motora $T_m = 0.04\text{s}$;

$K_a = 20$; $K_{tg} = 1 \frac{\text{V}}{\text{rad} \cdot \text{s}^{-1}}$; $R = 100\text{k}\Omega$; $C = 1\mu\text{F}$;

Nacrtati strukturnu blok šemu sistema.

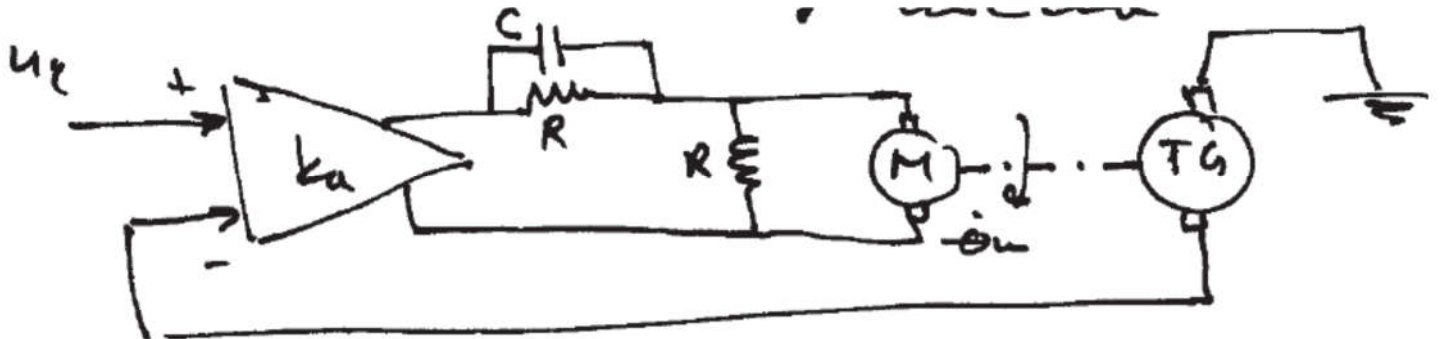


Rešenje:

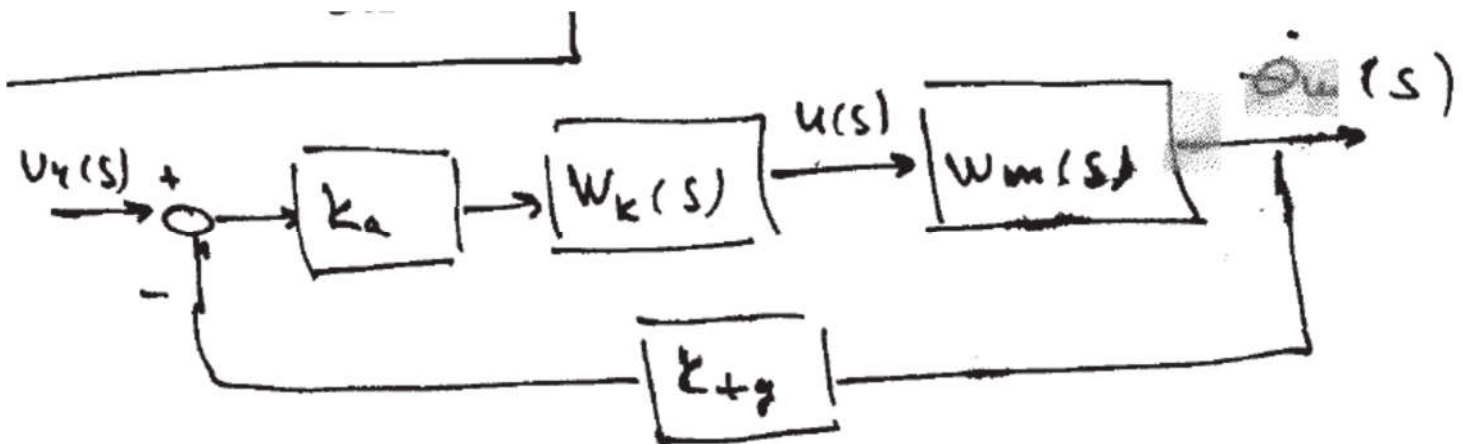

$$\text{Diferencijalni kompenzator: } W_k(s) = \frac{R}{\frac{R}{1+sCR} + R} = \frac{1+sCR}{2+sCR} = \frac{0.1s+1}{2(0.05s+1)} = \frac{s+10}{s+20}$$

$$\text{Motor jednosmerne struje: } W_m(s) = \frac{\dot{\theta}_m(s)}{U(s)} = \frac{k_m}{1+sT_m} = \frac{0.5}{1+s0.04}$$

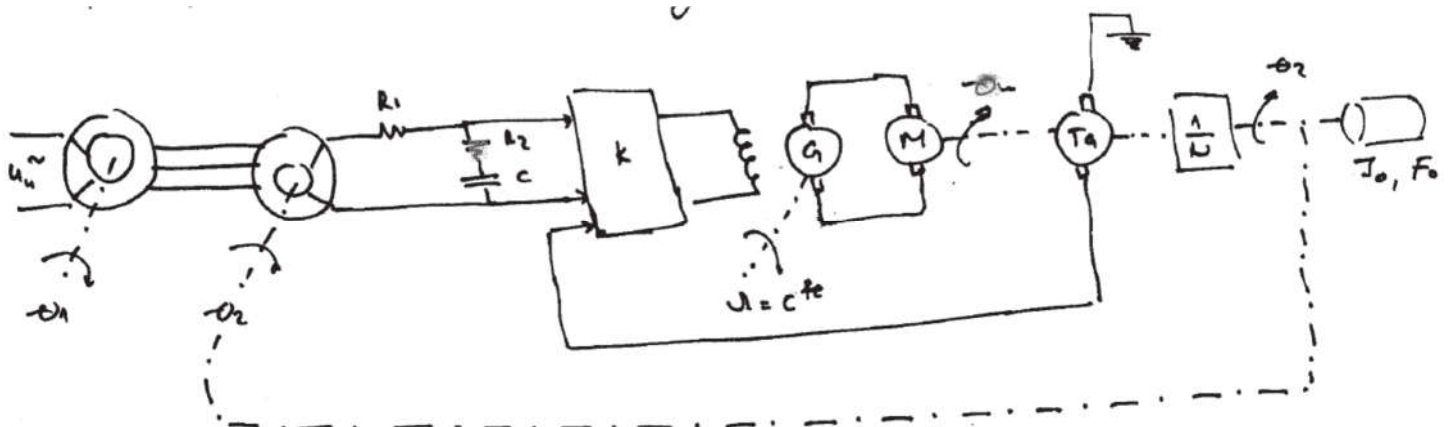6.10. Na slici je prikazana principska šema selsinskog pozicionog servosistema sa tahometarskom stabilizacionom povratnom spregom. Nacrtati strukturnu blok šemu i odrediti f-je prenosa elemenata u njoj.



Rešenje:

Transformatorska veza selsina:

$$u_s = K_s \sin(\theta_1 - \theta_2)$$

$$\text{za } \theta_1 - \theta_2 \text{ malo} \Rightarrow u_s = K_s (\theta_1 - \theta_2) \text{ jer je } \sin(\theta_1 - \theta_2) \approx \theta_1 - \theta_2$$

$$W_s = \frac{U_s(s)}{\theta_1(s) - \theta_2(s)} = K_s$$

$$\text{Integralni kompenzator: } W_k(s) = \frac{U_k(s)}{U_s(s)} = \frac{1 + sT_1}{1 + sT_2}; T_1 = R_2 C; T_2 = (R_1 + R_2) C;$$

$$\text{Pojačavač: } W_p(s) = \frac{U_p(s)}{U_e(s)} = K; U_e(s) = U_k(s) - U_{ig}(s)$$

Vard-Leonardova grupa:

$$W_{WLG}(s) = \frac{k}{s(1 + sT_1)(1 + sT_2)}$$

$$k = \frac{k_g k_{em}}{R_p [(R_r + R_g)F + k_{em} k_{me}]} \quad T_1 = \frac{L_p}{R_p} \quad T_2 = \frac{(R_r + R_g)J}{[(R_r + R_g)F + k_{em} k_{me}]}$$

$$F = F_m + \frac{F_o}{N^2}; J = J_m + \frac{J_o}{N^2}$$

$$\text{Reduktor: } W_R(s) = \frac{\theta_2(s)}{\theta_m(s)} = \frac{1}{N}$$

$$\text{Tahogenerator: } W_{ig}(s) = \frac{U_{ig}(s)}{\theta_m(s)} = sK_{ig}$$

